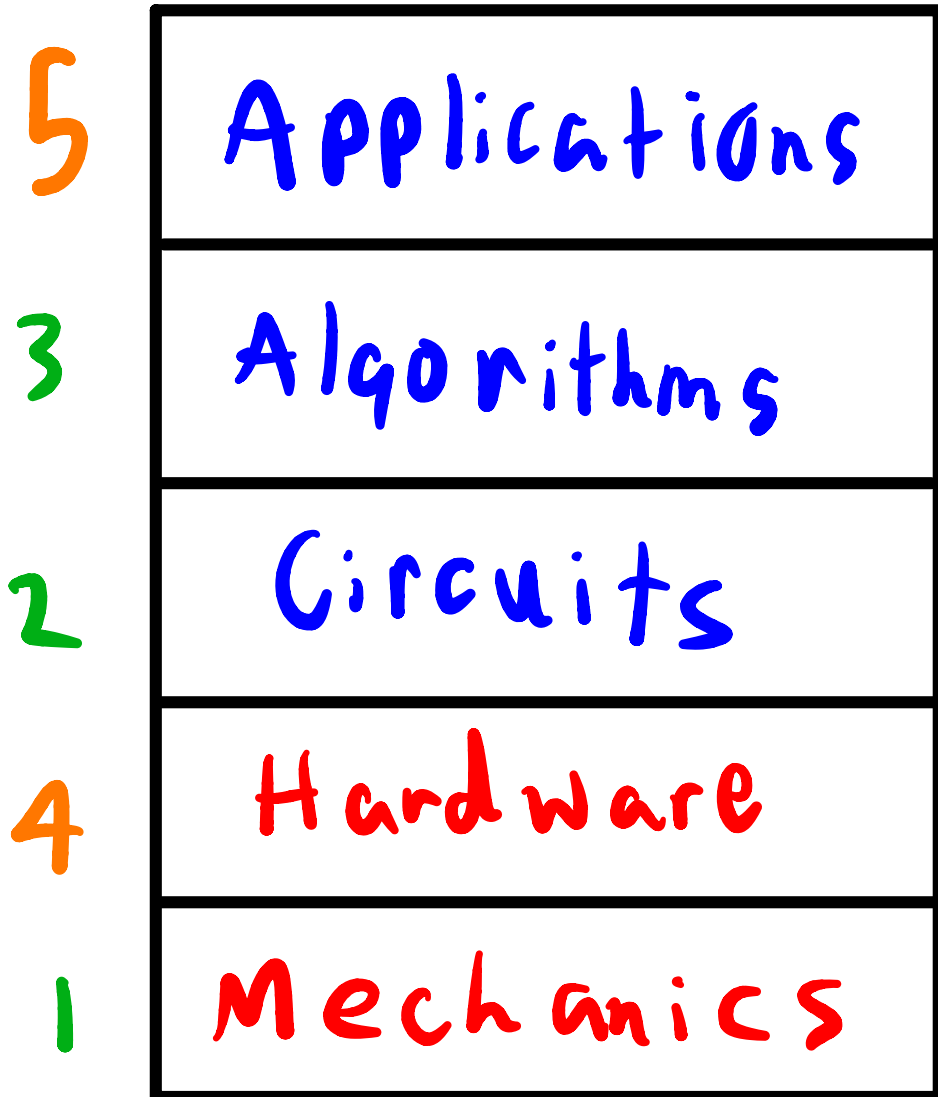




Quantum Circuits IV

The Quantum Computing Stack



Now Getting
our hands dirty
w/ circuits
Last Time
2+ qubits

States and Gates

Covered

$$|0\rangle = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$|1\rangle = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$|+\rangle = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$|-\rangle = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

$$X = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

$$Y = \begin{bmatrix} 0 & -i \\ i & 0 \end{bmatrix}$$

$$Z = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix}$$

$$H = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$

$$X |0\rangle = |1\rangle$$

$$X |1\rangle = |0\rangle$$


$$H |0\rangle = |+\rangle$$

$$H |1\rangle = |-\rangle$$


$$CNOT |b\rangle \otimes |a\rangle = |b \oplus a\rangle \otimes |a\rangle$$

$$\begin{array}{l} 1 \oplus 1 = 0 \\ 1 \oplus 0 = 1 \\ 0 \oplus 0 = 0 \end{array} \quad \sigma(=1)$$


Classical Gates

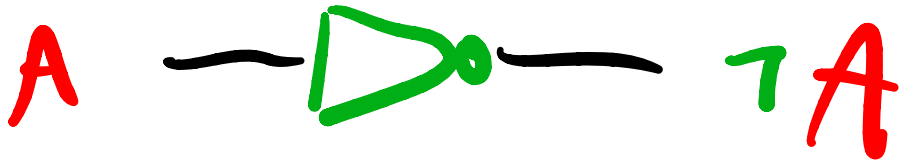


NOT

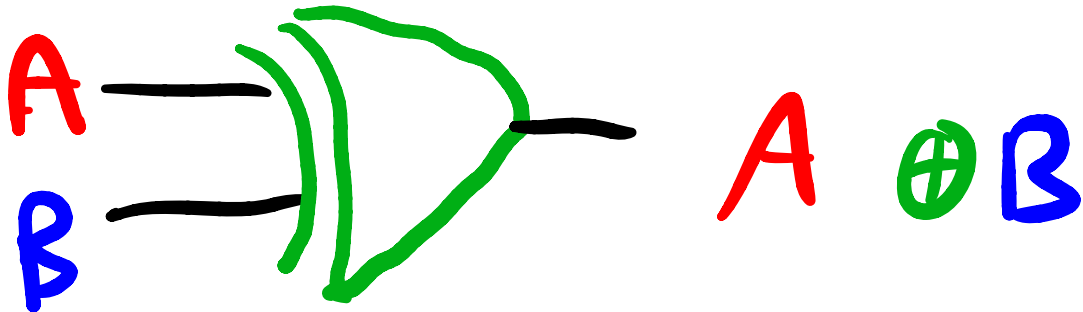

XOR

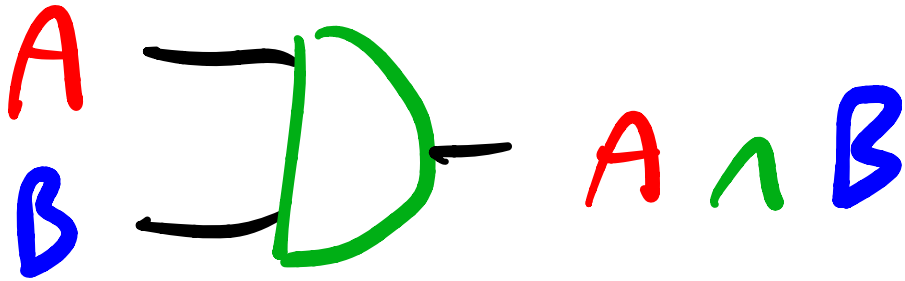


AND

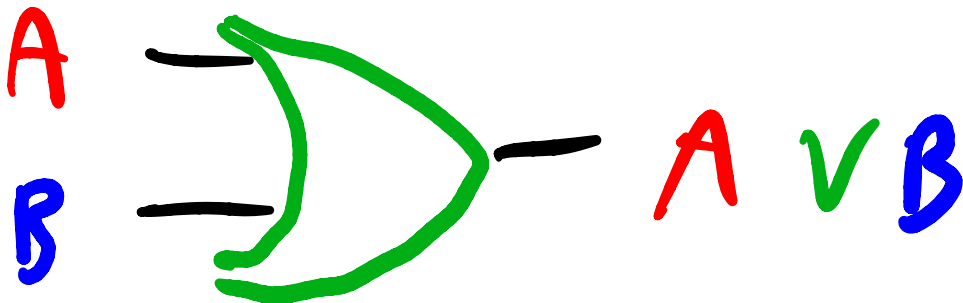


OR

NOT

<i>in</i>	<i>out</i>
0	1
1	0

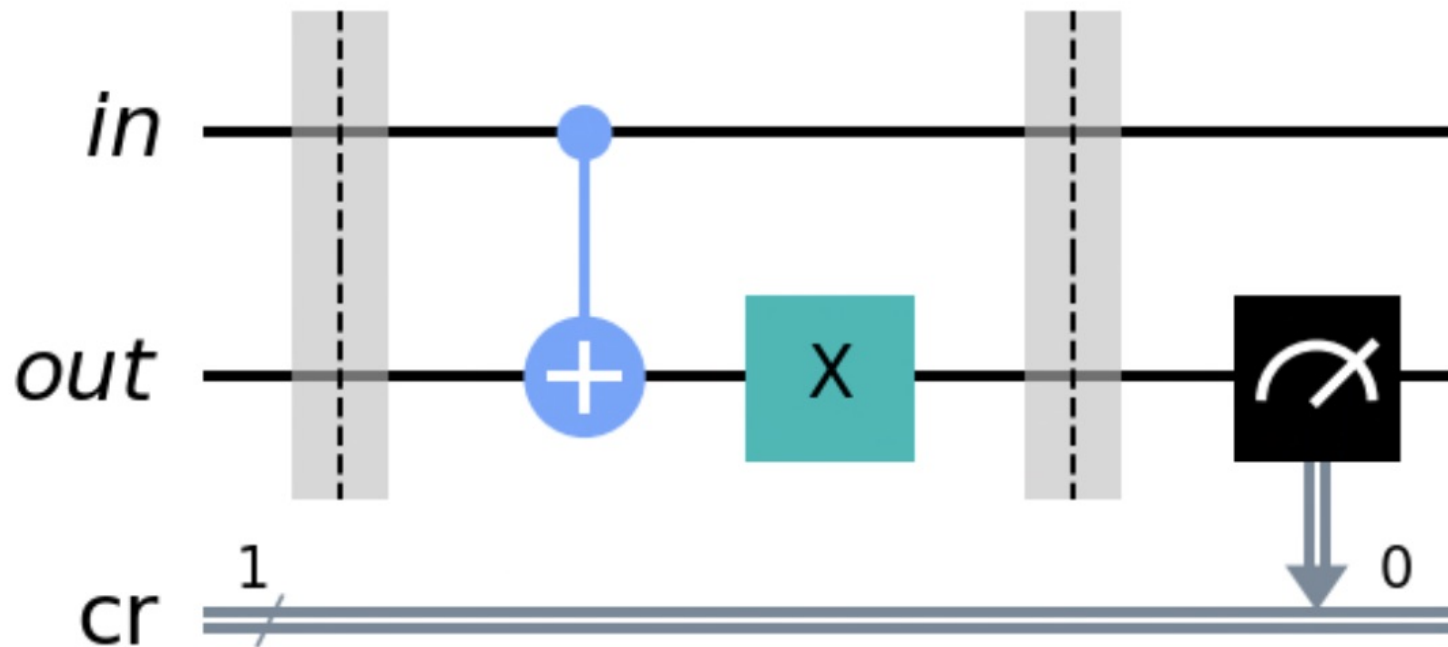

Reading
2 qubit
circuit

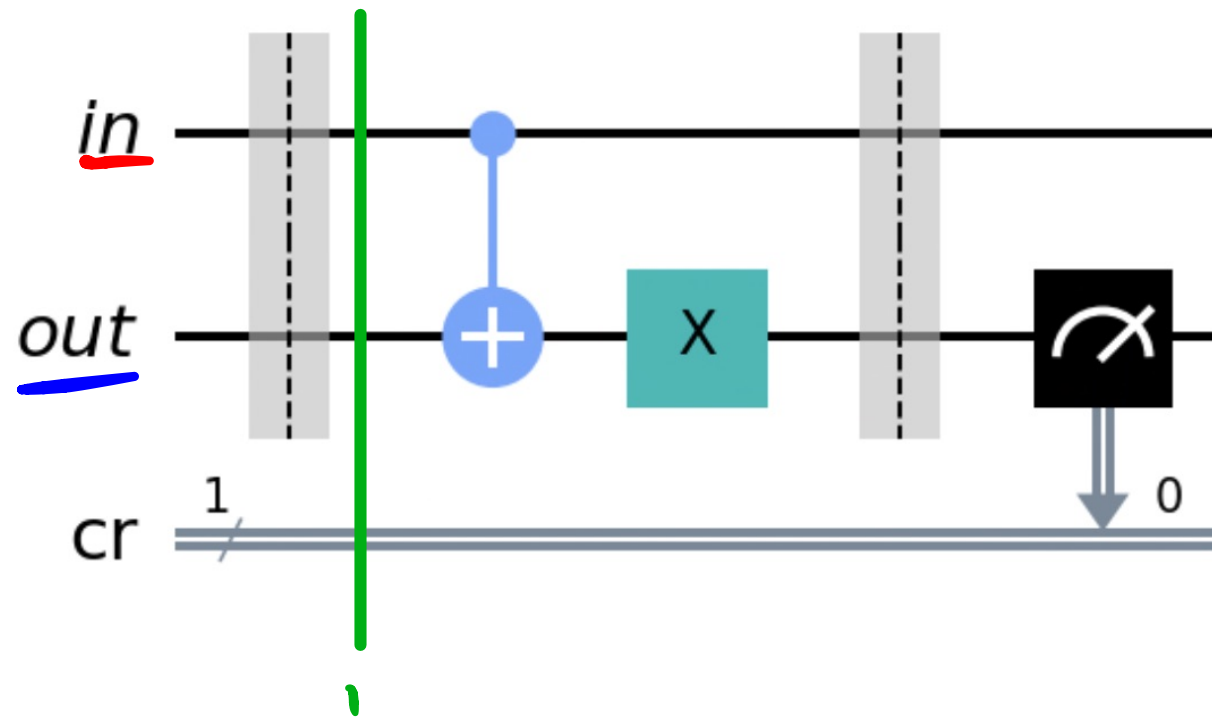


1:

convenient
notation ↓

$$|0\rangle \otimes |0\rangle = |00\rangle$$


Reading
2 qubit
circuit

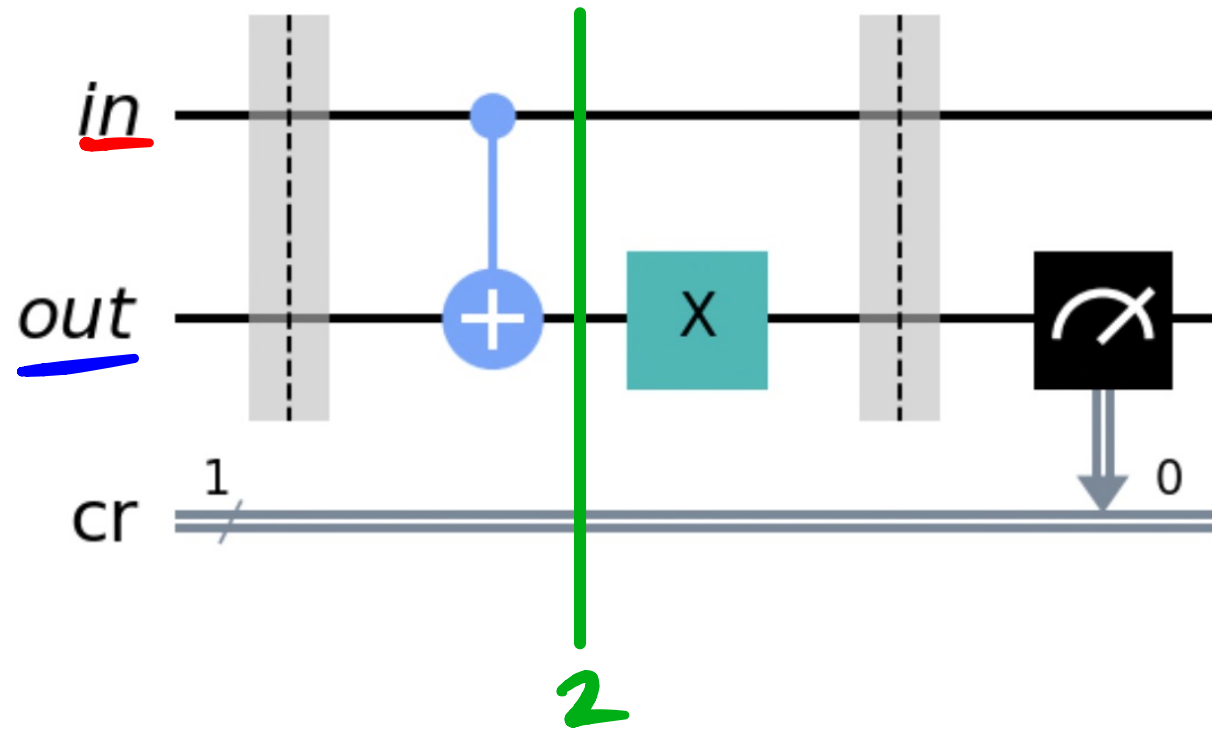

2:

$$\begin{aligned}
 \text{CNOT}(|0\rangle \otimes |0\rangle) &= |00\rangle \otimes |0\rangle \\
 &= |0\rangle \otimes |0\rangle
 \end{aligned}$$

Reading
2 qubit
circuit

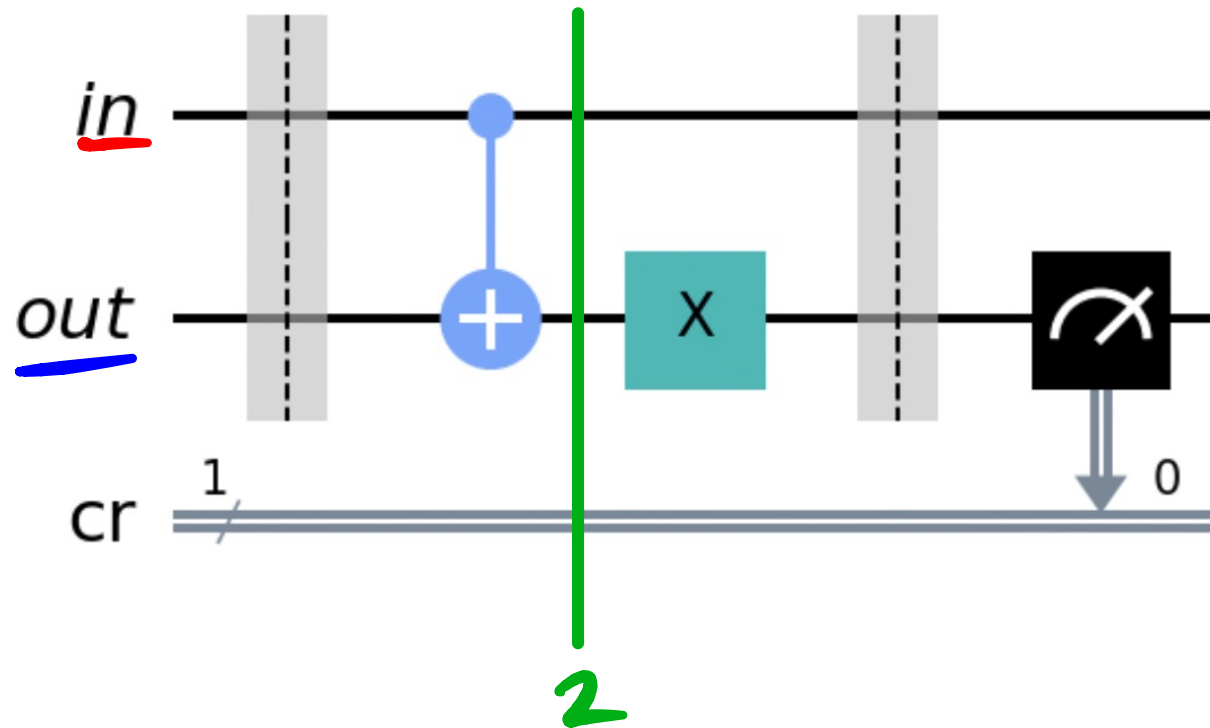


2:

$$\text{CNOT}(|0\rangle \otimes |0\rangle) = \begin{bmatrix} -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \otimes \begin{bmatrix} 1 \\ 0 \end{bmatrix} = |0\rangle \otimes |0\rangle$$


Reading
2 qubit
circuit

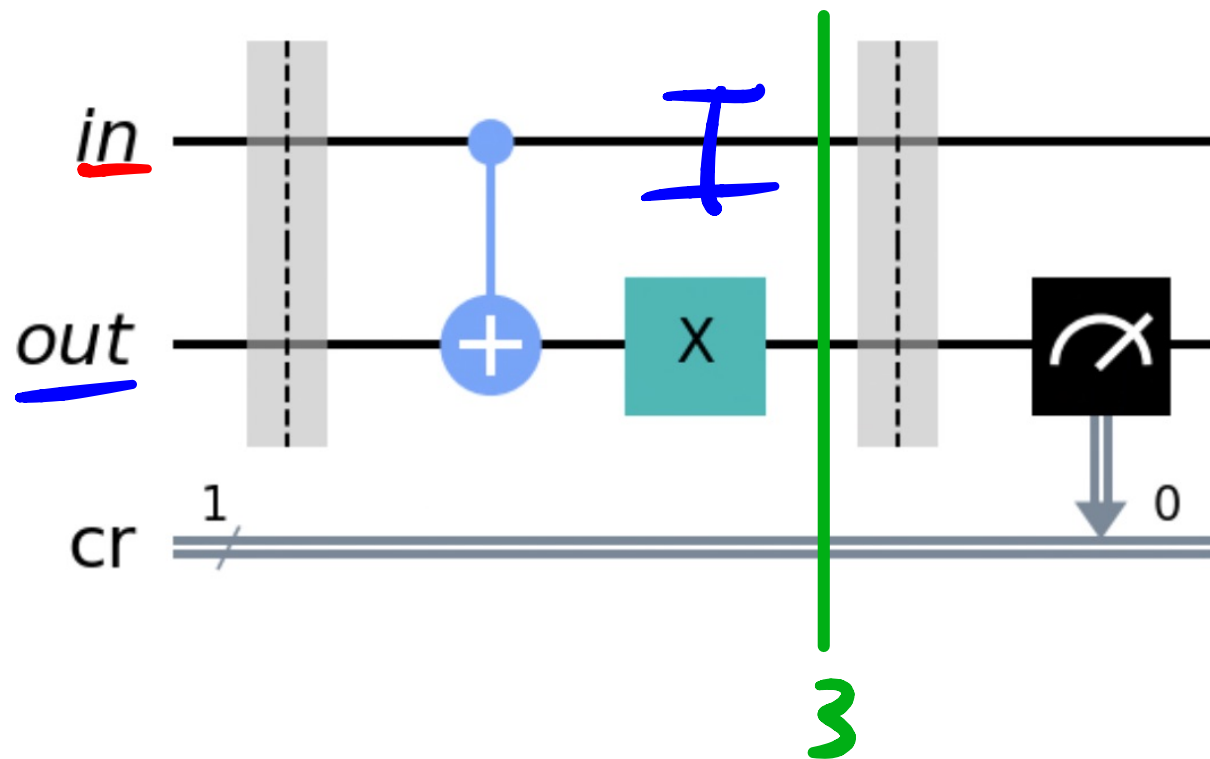

$$3: (X \otimes I) (|10\rangle \otimes |10\rangle)$$

$$= X|10\rangle \otimes |10\rangle = |11\rangle \otimes |10\rangle = |110\rangle$$

Reading
2 qubit
circuit

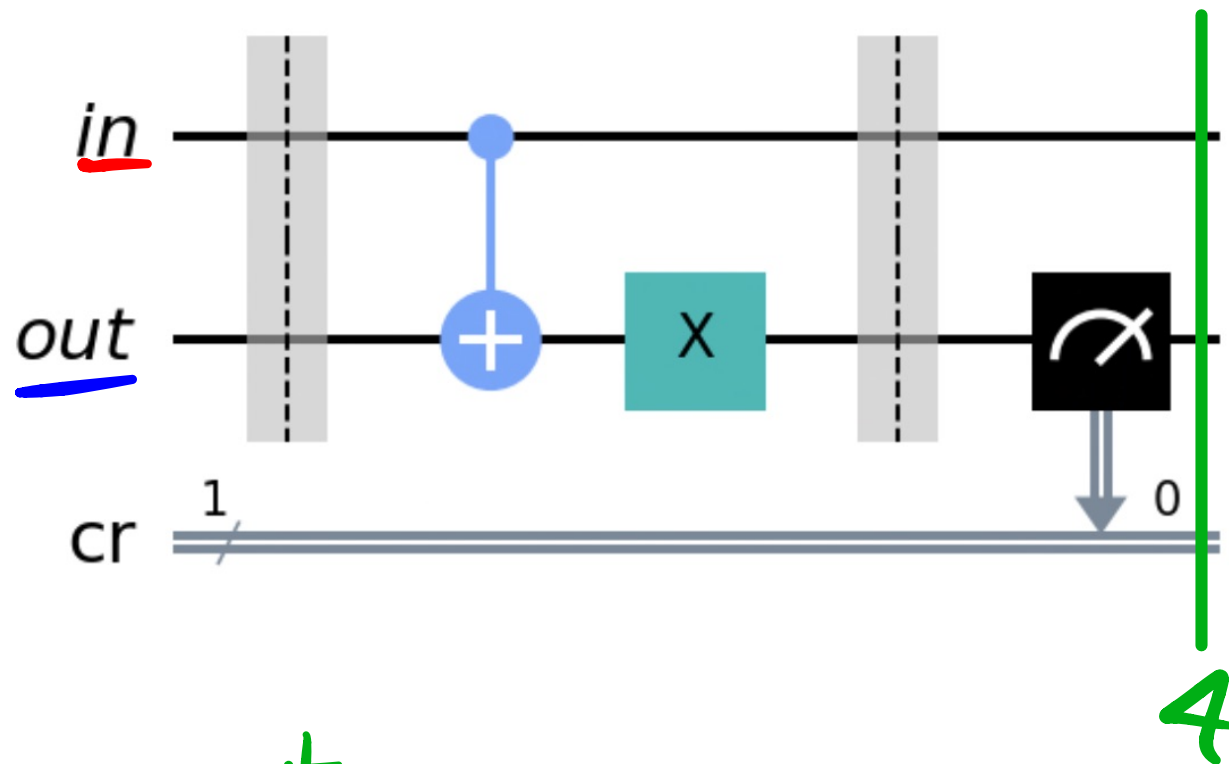

Measurement

$|1\rangle \otimes |0\rangle$


We only care to
measure out

0:

$$\langle 0 | 1 \rangle = 0$$

1:

$$\langle 1 | 1 \rangle = 1$$

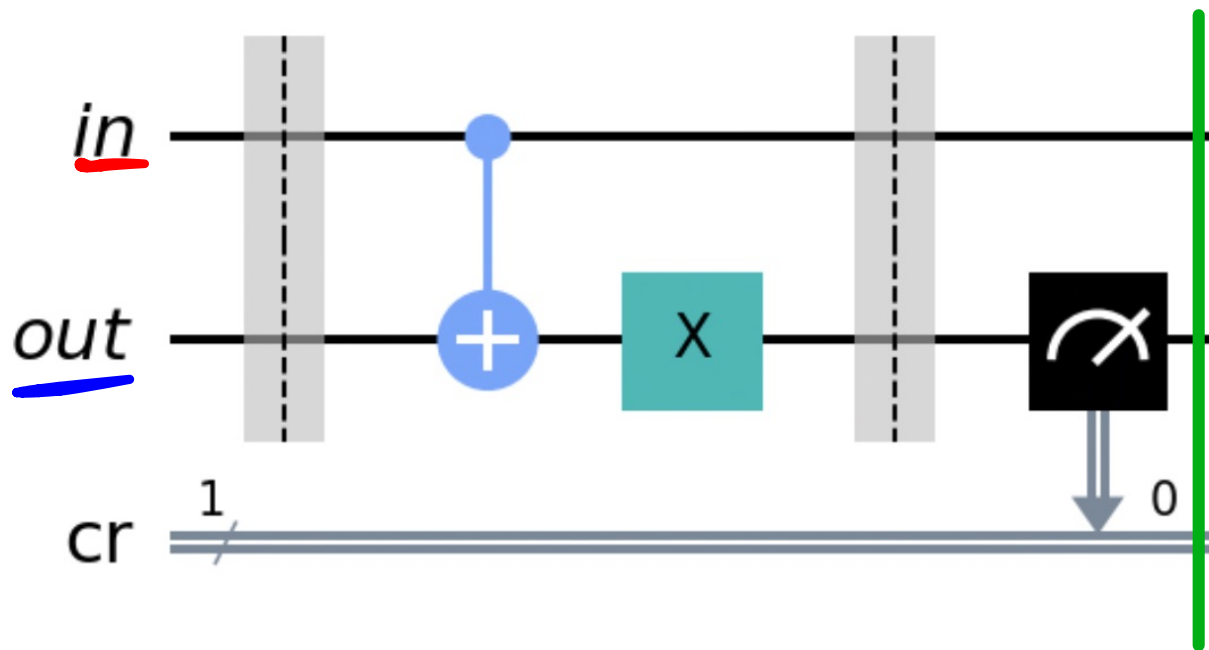

circuit = $(X \otimes I)$ CNOT


$$= \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

XOR


in_1	in_0	Out
0	0	0
0	1	1
1	0	1
1	1	0

CNOT $|0\rangle|1\rangle \rightarrow |1\rangle|1\rangle$

$$in_0 \oplus in_1 = Out$$

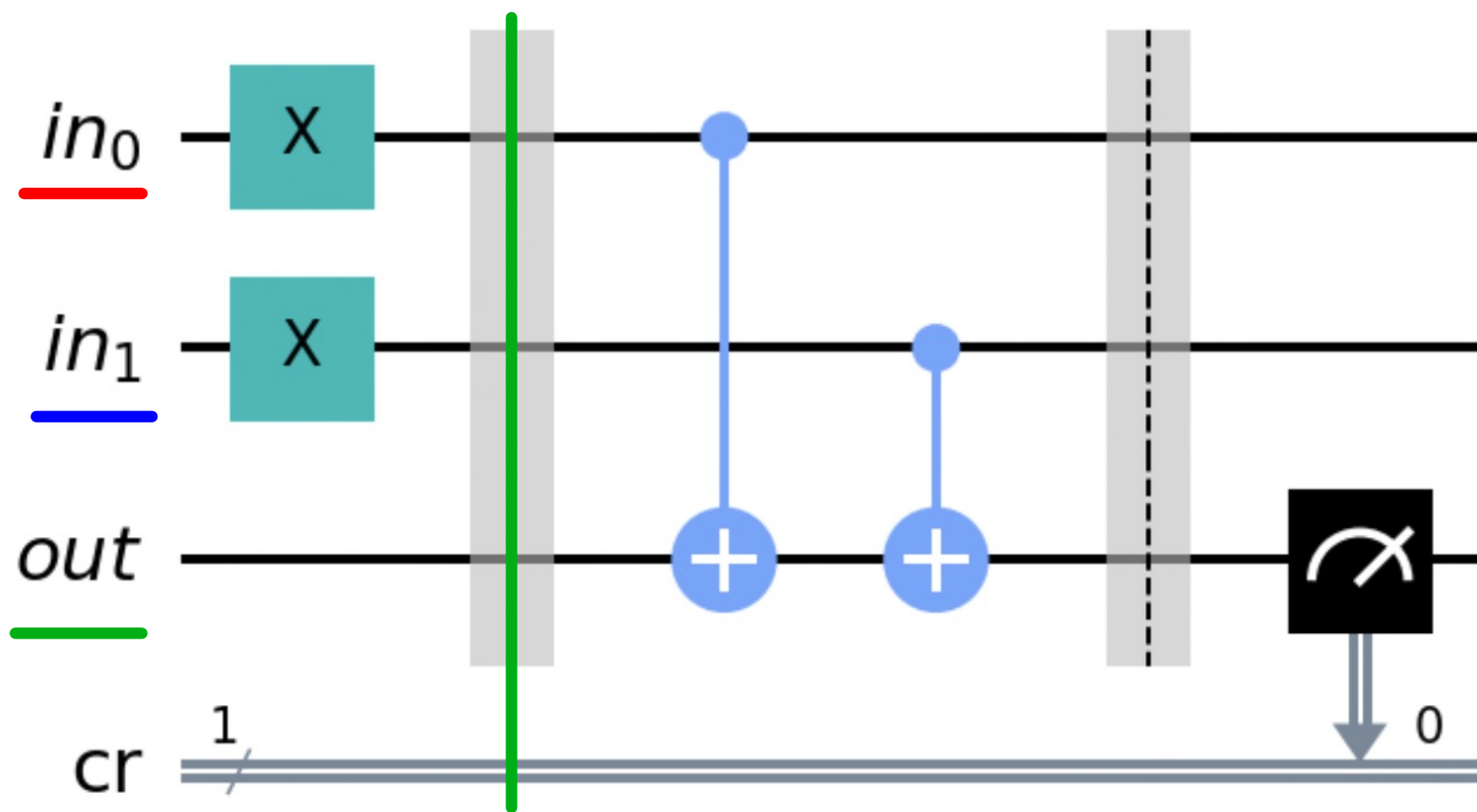


$|0\rangle \otimes |1\rangle \otimes |1\rangle$

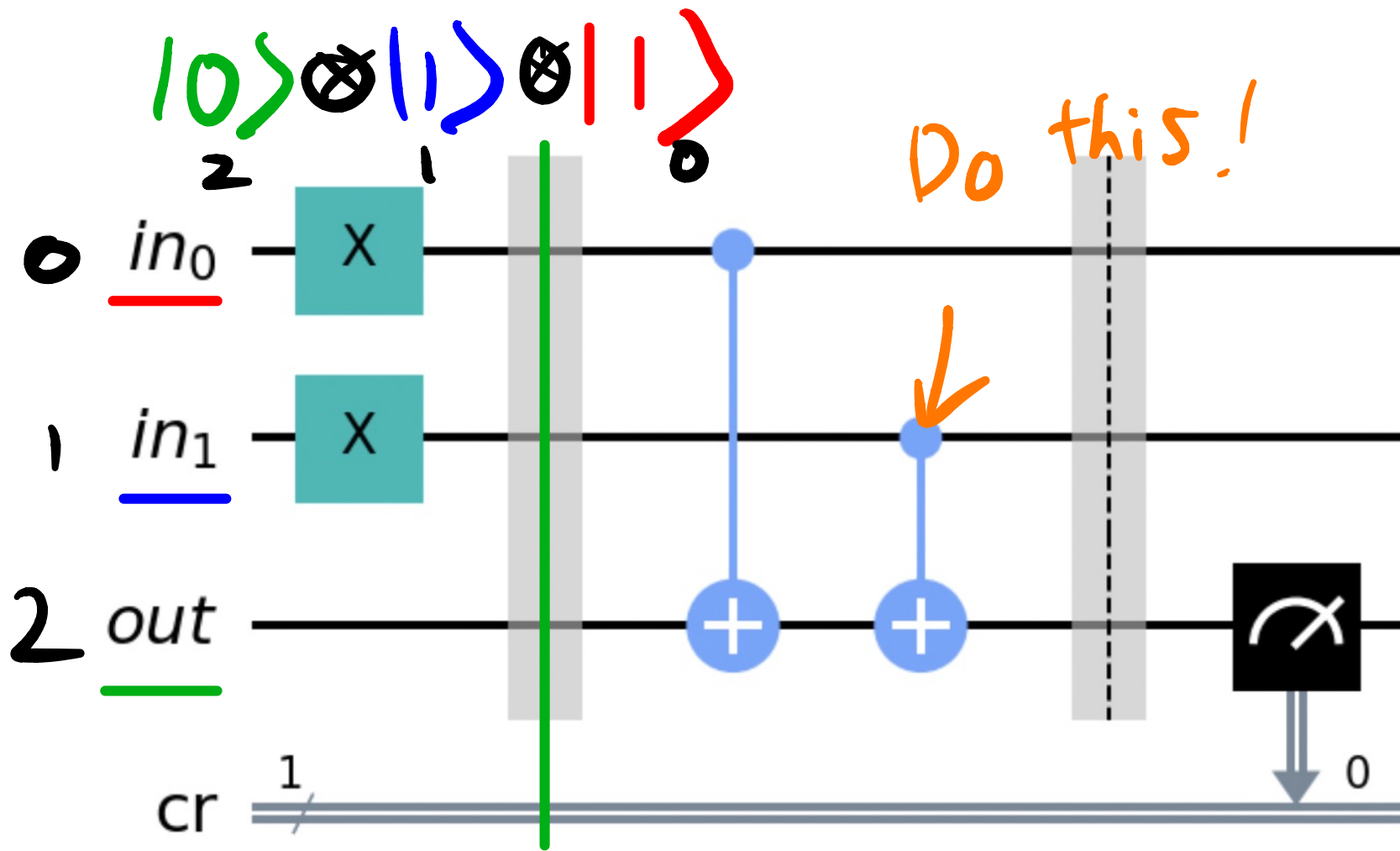

CNOT $(|0\rangle \otimes |1\rangle) = |0 \oplus 1\rangle \otimes |1\rangle$
 $= |11\rangle$


Now: $|11\rangle \otimes |11\rangle \otimes |11\rangle$

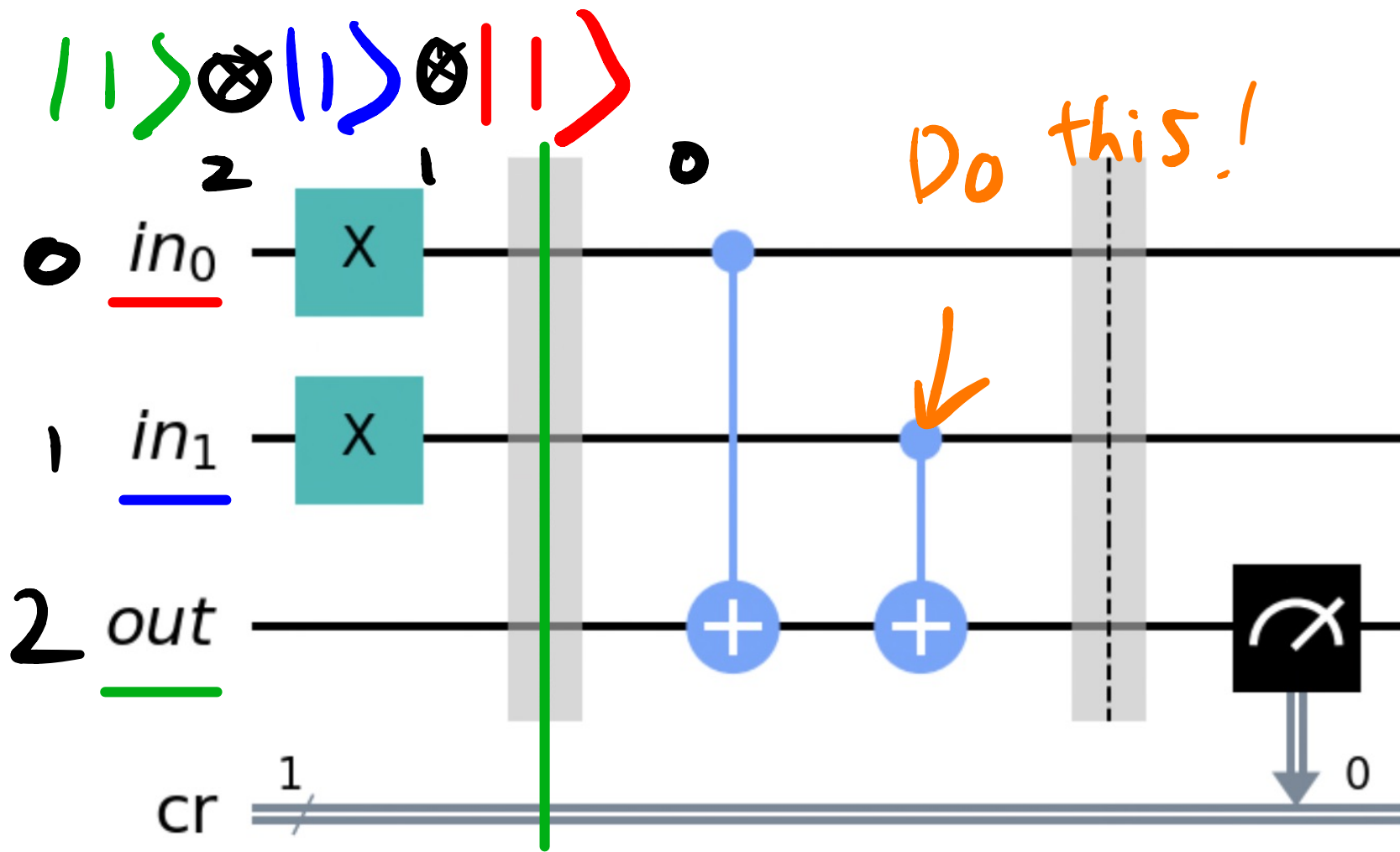

CNOT $(|1\rangle \otimes |1\rangle) = |1 \oplus 1\rangle \otimes |1\rangle$
 $= |0\rangle$

Now:

AND

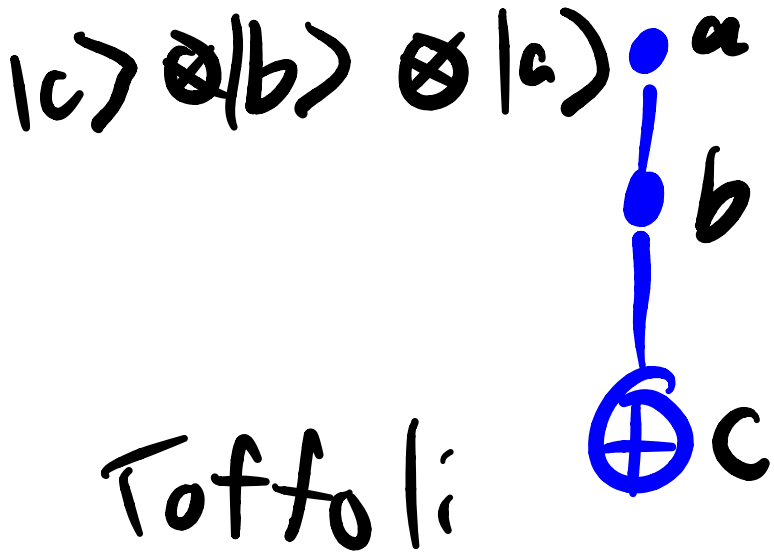

in_1	in_0	out
0	0	0
0	1	0
1	0	0
1	1	1

$$\text{Toffoli}(|c\rangle \otimes |b\rangle \otimes |a\rangle) = |c\rangle \otimes (a \wedge b) \otimes |b\rangle \otimes |a\rangle$$

OR

in_1	in_0	Out
0	0	0
0	1	1
1	0	1
1	1	1

Half-Adder

Binary


in_1	in_0	out_1	out_0
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$in_1 + in_0 = \underbrace{out_1}_{\text{And}} \underbrace{out_0}_{\text{XOR}}$$

Half-Adder Skeleton

States Gates Measurement

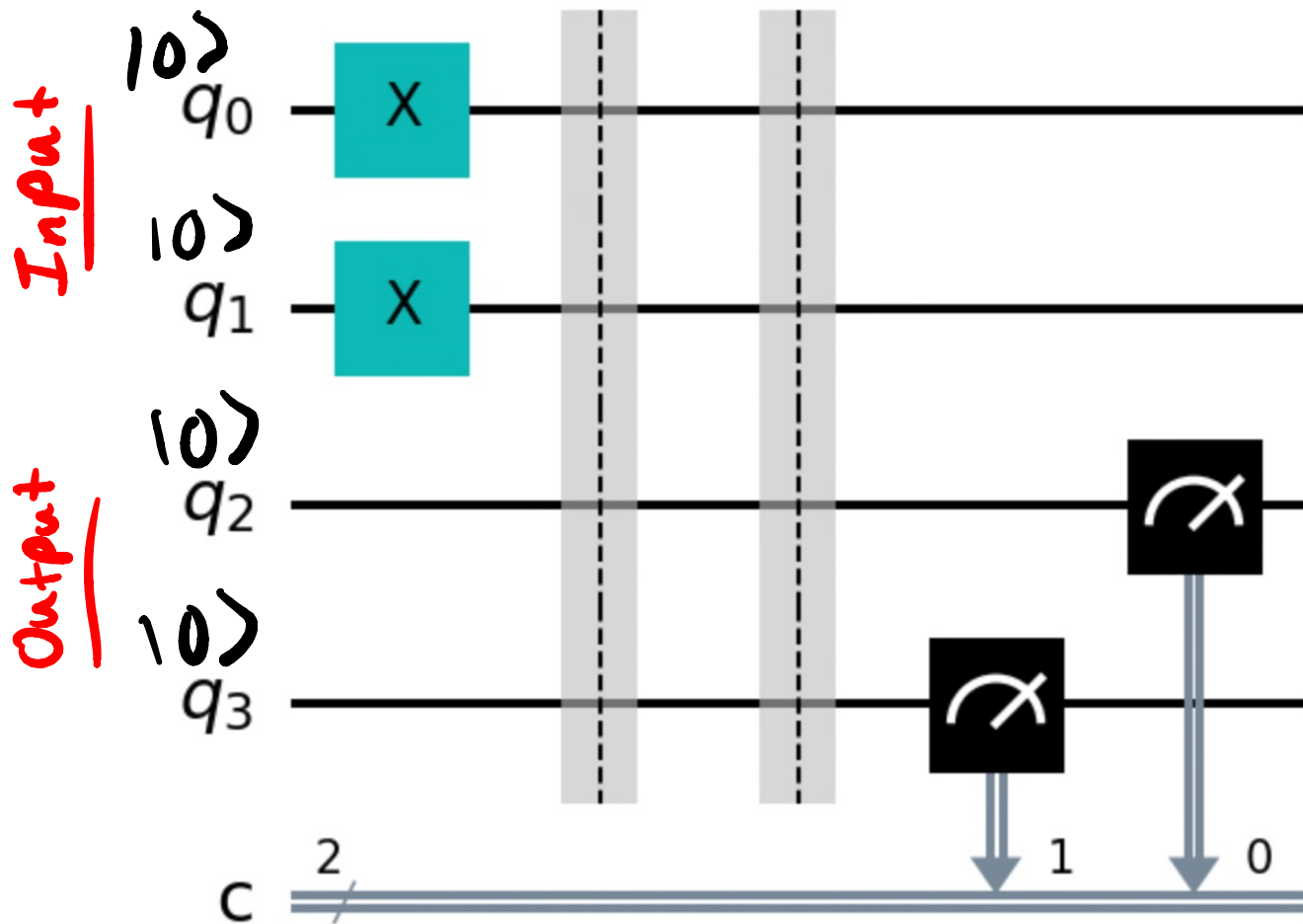Why are the 'X' gates in the states portion?





Keyword:

Totoro

Full - Adder

in_2	in_1	in_0	out_1	out_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1